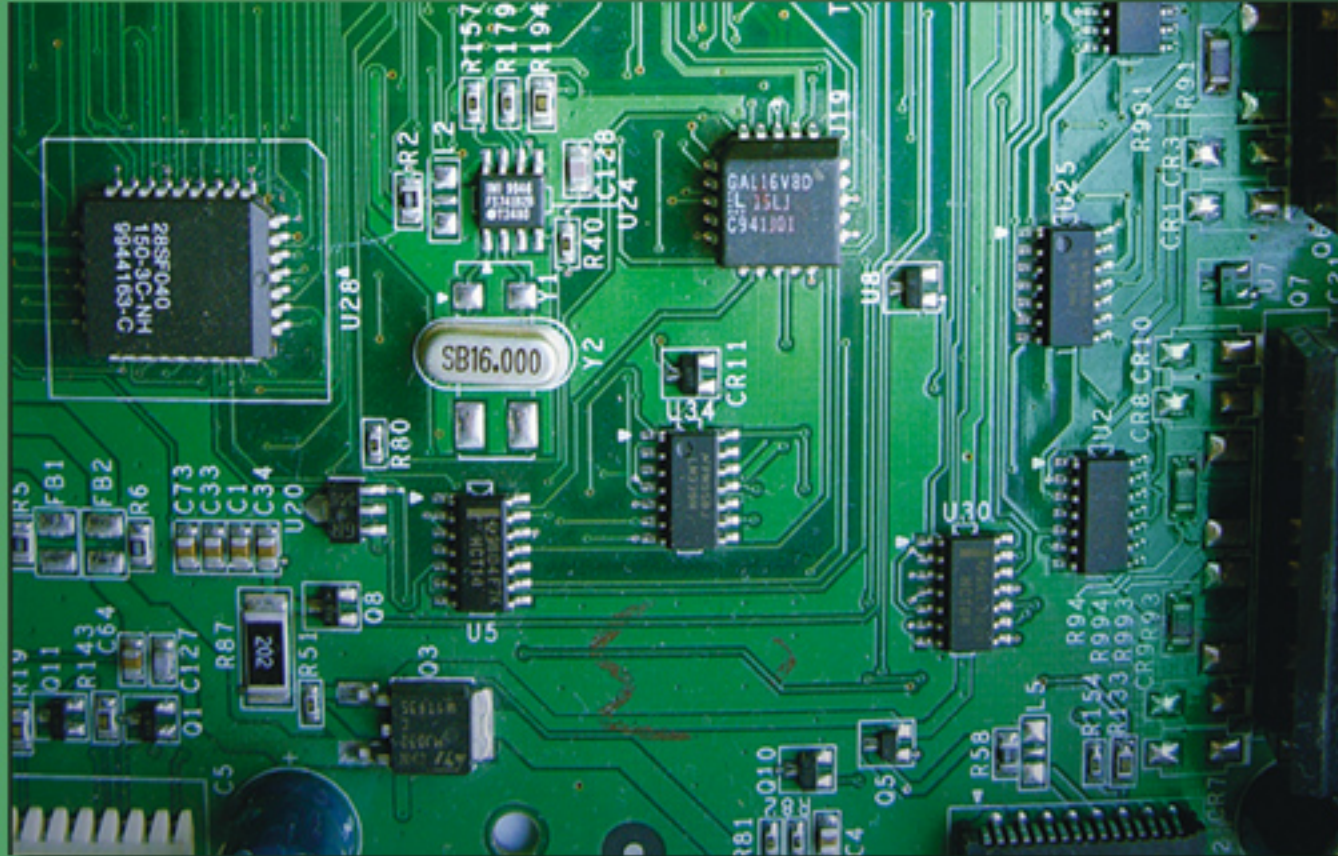


The Intel Microprocessors

8086/8088, 80186/80188, 80286, 80386, 80486 Pentium, Pentium Pro Processor, Pentium II, Pentium 4, and Core2 with 64-bit Extensions

Architecture, Programming, and Interfacing



EIGHTH EDITION

Barry B. Brey

PEARSON

Chapter 11: Basic I/O Interface

Introduction

- This chapter outlines some of the basic methods of **communications**, both **serial** and **parallel**, between humans or machines and the microprocessor.
- We first introduce the basic I/O interface and discuss **decoding** for I/O devices.
- Then, we provide detail on **parallel** and **serial** interfacing, both of which have a variety of applications.

Objectives

Upon completion of this lecture, you will be able to:

- Explain the operation of the basic input and output **interfaces**.
- Decode an 8-, 16-, and 32-bit I/O device so that they can be used at any I/O port address.
- Define **handshaking** and explain how to use it with I/O devices.

11–1 INTRO TO I/O INTERFACE

- I/O instructions (**IN**, **INS**, **OUT**, and **OUTS**) are explained.
- Also **isolated** (direct or I/O mapped I/O) and **memory-mapped** I/O, the basic **input** and **output interfaces**, and **handshaking**.
- Knowledge of these topics makes it easier to understand the **connection** and **operation** of the **programmable interface components** and **I/O techniques**.

The I/O Instructions

- One type of instruction **transfers information** to an I/O device (**OUT**).
- Another **reads** from an I/O device (**IN**).
- Instructions are also provided to transfer **s**trings of data between memory and I/O.
 - **INS** and **OUTS**, found except the 8086/8088

- Instructions that transfer data between an **I/O device** and the microprocessor's **accumulator** (AL, AX, or EAX) are called **IN** and **OUT**.
- The I/O address is stored in register DX as a 16-bit address or in the byte (p8) immediately following the **opcode** as an **8-bit address**.
 - Intel calls the **8-bit** form (p8) a **fixed address** because it is stored with the instruction, usually in a ROM
- The **16-bit address** is called a **variable address** because it is stored in a DX, and then used to address the I/O device.

Other instructions that use DX to address I/O are the **INS** and **OUTS** instructions.

- I/O ports are **8 bits** in width.
 - a **16-bit port** is actually **two** consecutive **8-bit ports** being addressed
 - a **32-bit I/O port** is actually **four 8-bit ports**

- When data are transferred using **IN** or **OUT**, the I/O address, (**port number** or simply port), appears on the address bus.
- External I/O interface decodes the **port** number in the same manner as a memory address.
 - the 8-bit fixed **port number** (p8) appears on address bus connections A_7 – A_0 with bits A_{15} – A_8 equal to 00000000_2
 - connections above A_{15} are **undefined** for I/O instruction

- The 16-bit variable **port number** (DX) appears on address connections $A_{15}-A_0$.
- The first **256 I/O port** addresses (00H–FFH) are accessed by both fixed and variable I/O instructions.
 - any I/O address from 0100H to FFFFH is only accessed by the variable I/O address
- In a **PC computer**, all **16 address bus bits** are decoded with locations **0000H–03FFH**.
 - used for I/O inside the PC on the **ISA** (**industry standard architecture**) bus

- **INS** and **OUTS** instructions address an I/O device using the DX register.
 - but do not transfer data between accumulator and I/O device as do the IN/OUT instructions
 - Instead, they **transfer data** between memory and the I/O device
- Pentium 4 and Core2 operating in the **64-bit mode** have the same I/O instructions.
- There are **no 64-bit I/O instructions** in the 64-bit mode.
 - most I/O is **still 8 bits** and likely will remain so

instructions.

Instruction	Data Width	Function
IN AL, p8	8	A byte is input into AL from port p8
IN AX, p8	16	A word is input into AX from port p8
IN EAX, p8	32	A doubleword is input into EAX from port p8
IN AL, DX	8	A byte is input into AL from the port addressed by DX
IN AX, DX	16	A word is input into AX from the port addressed by DX
OUT p8, AL	8	A byte is output from AL into port p8
OUT p8, AX	16	A word is output from AX into port p8
OUT p8, EAX	32	A doubleword is output from EAX into port p8
OUT DX, AL	8	A byte is output from AL into the port addressed by DX
OUT DX, AX	16	A word is output from AX into the port addressed by DX
OUT DX, EAX	32	A doubleword is output from EAX into the port addressed by DX
OUTSB	8	A byte is output from the data segment memory location addressed by SI into the port addressed by DX, then SI = SI ± 1
OUTSW	16	A word is output from the data segment memory location addressed by SI into the port addressed by DX, then SI = SI ± 2
OUTSD	32	A doubleword is output from the data segment memory location addressed by SI into the port addressed by DX, then SI = SI ± 4

Isolated and Memory-Mapped I/O




- Two different methods of interfacing I/O: **isolated I/O** and **memory-mapped I/O**.
- In isolated I/O, the IN, INS, OUT, and OUTS transfer data between the microprocessor's **accumulator** or memory and the **I/O device**.
- In memory-mapped I/O, any instruction that references memory can accomplish the transfer.
- The PC does not use memory-mapped I/O.

Isolated I/O

- The most common I/O transfer technique used in the **Intel-based system** is **isolated I/O**.
 - *isolated* describes how I/O locations are isolated from memory in a separate I/O address space
- Addresses for isolated I/O devices, called **ports**, are separate from memory.
- Because the ports are separate, the user can expand the memory to its full size without using any of memory space for I/O devices.

- A disadvantage of isolated I/O is that data transferred between I/O and microprocessor must be accessed by the IN, INS, OUT, and OUTS instructions.
- **Separate control signals** for the I/O space are developed (using M/\overline{IO} and W/\overline{R}), which indicate an I/O read (\overline{IORC}) or an I/O write (\overline{RD}) operation.
- These signals indicate an **I/O port address**, which appears on the address bus, is used to **select** the I/O device.

Figure 11–1 The memory and I/O maps for the 8086/8088 microprocessors. (a) **Isolated I/O**. (b) **Memory-mapped I/O**.

   


- in the PC, isolated I/O ports are used to control peripheral devices
- an **8-bit port address** is used to access devices located on the system board, such as the timer and **keyboard** interface
- a **16-bit port** is used to access serial and parallel ports, **video** and **disk drive** systems

Memory-Mapped I/O

- Memory-mapped I/O does not use the IN, INS, OUT, or OUTS instructions.
- It uses any instruction that transfers data between the microprocessor and memory.
 - treated as a **memory location** in memory map
- **Advantage** is any memory transfer instruction can access the I/O device.
- **Disadvantage** is a portion of memory system is used as the I/O map.
 - **reduces memory available** to applications

Personal Computer I/O Map

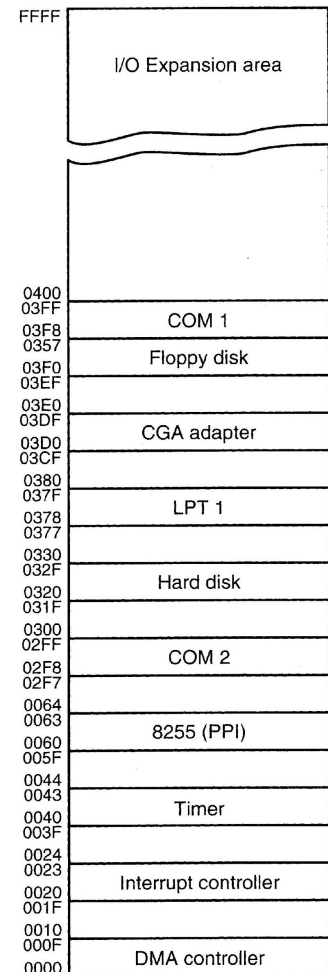

- the PC uses part of **I/O map** for dedicated functions, as shown here
- I/O space between **ports 0000H and 03FFH** is normally reserved for the system and **ISA bus**
- ports at **0400H–FFFFH** are generally available for user applications, main-board functions, and the **PCI bus**
- 80287 coprocessor uses **00F8H–00FFH**, so Intel reserves I/O ports 00F0H–00FFH

Figure 11–2 I/O map of a personal computer illustrating many of the fixed I/O areas.


Basic Input and Output Interfaces

- The basic **input device** is a set of **three-state buffers**.
- The basic **output device** is a set of **data latches**.
- The term **IN** refers to moving data *from the I/O device into the microprocessor* and
- The term **OUT** refers to moving data *out of the microprocessor to the I/O device*.

The Basic Input Interface

- **Three-state buffers** are used to construct the 8-bit input port depicted in Figure 11–3.
- External TTL data are connected to the inputs of the buffers.
 - buffer outputs connect to the data bus
- The circuit of allows the processor to read the contents of the eight switches that connect to any **8-bit** section of the data bus when the select signal becomes a logic 0.

Figure 11–3 The basic **input interface** illustrating the connection of eight switches. Note that the 74ALS244 is a **three-state buffer** that controls the application of the switch data to the data bus.

 


- When the IN instruction executes, **contents** of the switches **copy** to the **AL register**.
- This basic input circuit is not optional and must appear any time input data are interfaced to the microprocessor.
- Sometimes it appears as a discrete part of the circuit, as shown in Figure 11–3.
 - also built into a programmable I/O devices
- **Sixteen-** or **32-bit data** can also be interfaced but is not nearly as common as **8-bit data**.

The Basic Output Interface

- Receives data from the processor and usually must hold it for some external device.
 - latches or flip-flops, like buffers in the input device, are often built into the I/O device
- Fig 11–4 shows how **eight** light-emitting diodes (LEDs) connect to the processor through a set of **eight** data latches.
- The latch stores the number output by the microprocessor from the data bus so that the **LEDs** can be **lit** with any 8-bit binary number.

Figure 11–4 The basic **output** interface connected to a set of LED displays.

 

- Latches **hold** the data because when the processor executes an OUT, data are only present on the data bus for less than $1.0\ \mu\text{s}$.
 - the viewer would never see the LEDs illuminate
- When the OUT executes, data from AL, AX, or EAX transfer to the latch via the data bus.
- Each time the OUT executes, the $\overline{\text{SEL}}$ signal activates, **capturing data** to the latch.
 - data are held until the next OUT
- When the output instruction is executed, data from the **AL register** appear on the LEDs.

Handshaking

- Many I/O devices accept or release information **slower** than the microprocessor.
- ✓ A method of I/O control called **handshaking** or **polling**, synchronizes the I/O device with the microprocessor.
- An example is a parallel printer that prints a few hundred characters per second (**CPS**).
- The processor can send data much **faster**.
 - a way to slow the microprocessor down to match speeds with the printer must be developed

- Fig 11–5 illustrates typical input and output connections found on a printer.
 - data transfers via data connections (D_7 – D_0)
- ASCII data are placed on D_7 – D_0 , and a pulse is then applied to the \overline{STB} connection.
- ✓ – **BUSY** indicates the printer is busy
- ✓ – **STB** is a clock pulse used to send data to printer
- The **strobe signal** sends or clocks the data into the printer so that they can be printed.
 - as the printer receives data, it places logic 1 on the **BUSY** pin, indicating it is printing data

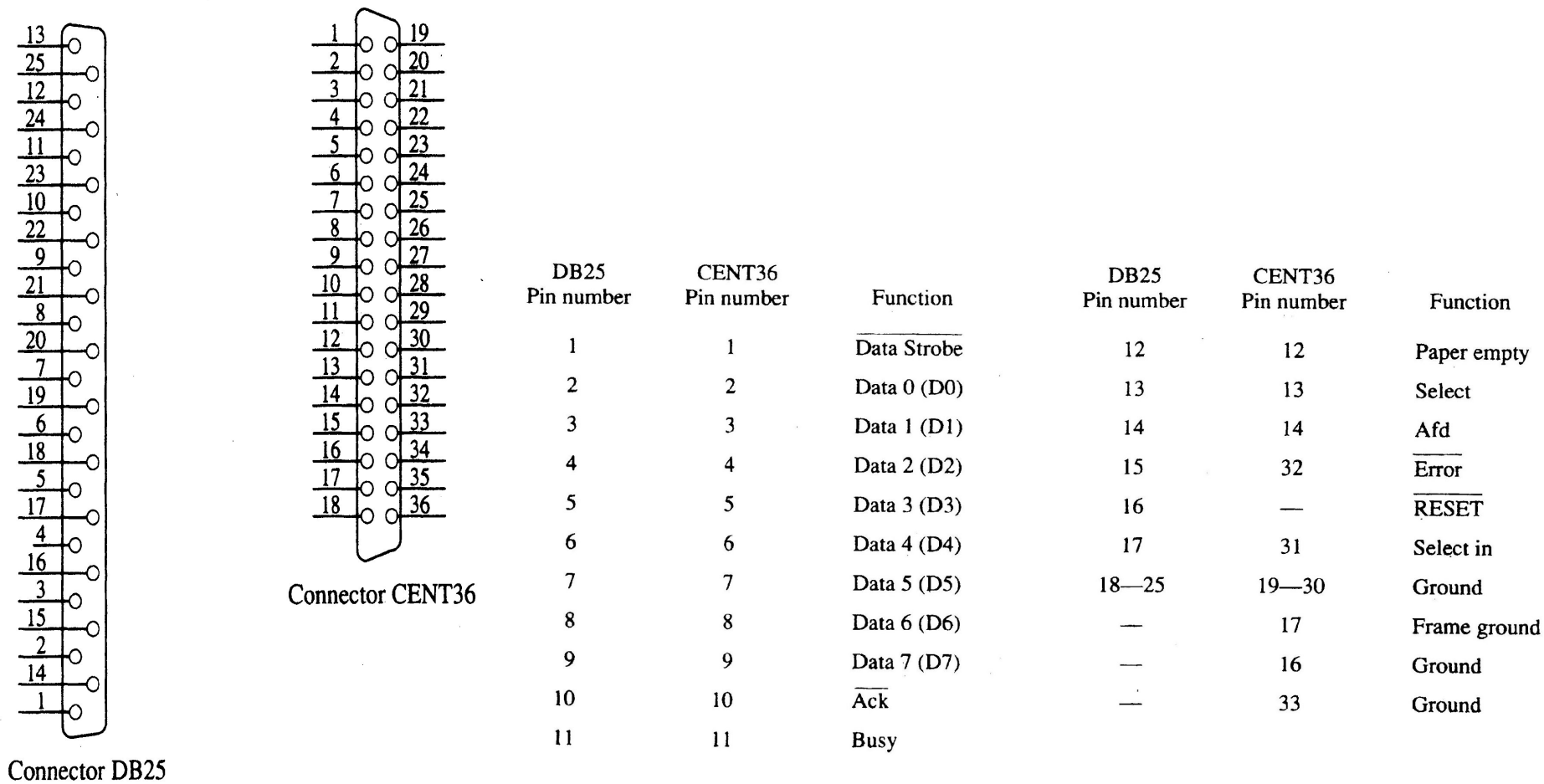


FIGURE 11-5 The DB25 connector found on computers and the Centronics 36-pin connector found on printers for the Centronics parallel printer interface.

- The software **polls** or tests the **BUSY** pin to decide whether the printer is busy.
 - If the **printer** is **busy**, the **processor waits**
 - if not, the next ASCII character goes to the printer
- This process of interrogating the printer, or any asynchronous device like a printer, is called **handshaking** or **polling**.

• **EXAMPLE 11-1**

- An assembly language procedure that prints the ASCII contents of BL.

PRINT PROC NEAR

.REPEAT ;test the busy flag

IN AL, BUSY

TEST AL, BUSY_BIT

.UNTIL ZERO

MOV AL, BL ;position data in AL

OUT PRINTER, AL ;print data

RET


PRINT ENDP

Input Devices

- Input devices are already TTL and **compatible**, and can be connected to the microprocessor and its interfacing components.
 - or they are **switch-based**
- Switch-based devices are either open or connected; These are not TTL levels.
 - TTL levels are a logic 0 (0.0 V–0.8 V)
 - or a logic 1 (2.0 V–5.0 V)
- Using **switch-based device** as TTL-compatible input requires conditioning applied.

- Fig 11–6 shows a **toggle switch** properly connected to function as an input device.
- A **pull-up resistor** ensures when the switch is open, the output signal is a logic 1.
 - when the switch is closed, it connects to ground, producing a valid logic 0 level
- A **standard range** of values for **pull-up** resistors is between 1K Ohm and 10K Ohm.

Figure 11–6 A single-pole, single-throw switch interfaced as a TTL device.

 


Output Devices ✓


- Output devices are **more diverse** than input devices, but many are interfaced in a **uniform** manner.
- Before an output device can be interfaced, we must understand voltages and currents from the microprocessor or TTL interface.
- Voltages are **TTL-compatible** from the microprocessor of the interfacing element.
 - logic 0 = 0.0 V to 0.4 V ✓
 - logic 1 = 2.4 V to 5.0 V ✓

- Currents for a processor and many interfacing components are less than for standard TTL.
 - Logic 0 = 0.0 to 2.0 mA
 - logic 1 = 0.0 to 400 μ A
- Fig 11–8 shows how to interface a simple LED to a microprocessor peripheral pin.
 - a transistor driver is used in 11–8(a)
 - a TTL inverter is used in 11–8(b)
- The TTL inverter (**standard version**) provides up to **16 mA** of current at a logic 0 level
 - more than enough to drive a **standard LED**

Figure 11–8 Interfacing an LED: (a) using a transistor and (b) using an inverter.

 

(a)

 

(b)

- TTL input signal has minimum value of 2.4 V
- Drop across emitter-base junction is 0.7 V.
- The difference is 1.7 V
 - the voltage drop across the resistor
- The value of the resistor is $1.7 \text{ V} \div 0.1 \text{ mA}$ or 17K Ω .
 - as 17K Ω is not a standard value, an 18K Ω resistor is chosen

- In 11–8(a), we elected to use a switching transistor in place of the TTL buffer.
 - 2N2222 is a good low-cost, general-purpose switching transistor with a minimum gain of 100
 - collector current is 10 mA; so base current will be 1/100 of collector current of 0.1 mA
- To determine the value of the base current–limiting resistor, use the 0.1 mA base current and a voltage drop of 1.7 V across the base **current–limiting resistor**.

- Suppose we need to interface a 12 V DC 1A motor to the microprocessor.

✍ We cannot use a TTL inverter:

- 12 V signal would burn out the inverter
- current far exceeds 16 mA inverter maximum

✍ We cannot use a 2N2222 transistor:

- maximum current is 250 mA to 500 mA, depending on the package style chosen


- The solution is to use a Darlington-pair, such as a TIP120.

- costs 25¢, can handle 4A current with heat sink

- Fig 11–9 illustrates a motor connected to the Darlington-pair with a minimum current gain of 7000 and a maximum current of 4A.
- Value of the bias resistor is calculated exactly the same as the one used in the LED driver.
- The current through the resistor is 1.0 A ÷ 7000, or about 0.143 mA.
- Voltage drop is 0.9 V because of the two diode drops (base/emitter junctions).
- The value of the bias resistor is 0.9 V ÷ 0.143 mA or 6.29K Ω .

Figure 11–9 A DC motor interfaced to a system by using a Darlington-pair.

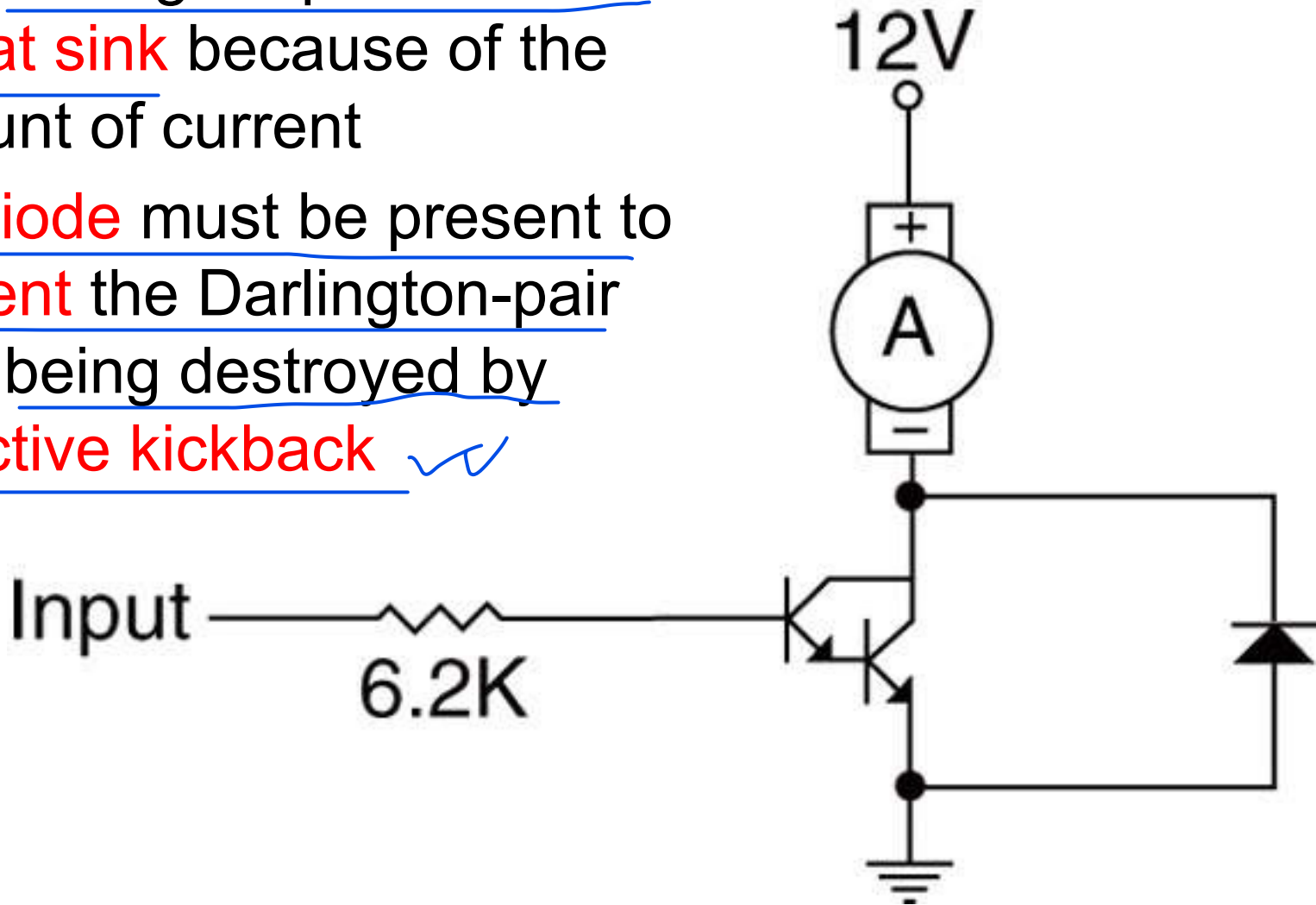- The Darlington-pair must use a heat sink because of the amount of current
- the diode must be present to prevent the Darlington-pair from being destroyed by inductive kickback ✓✓



11–2 I/O PORT ADDRESS DECODING

- Very **similar** to memory address decoding, especially for memory-mapped I/O devices.
- The difference between memory decoding and isolated I/O decoding is the number of address pins connected to the decoder.
- In the personal computer system, we always decode all **16 bits of the I/O port address**.

Decoding 8-Bit I/O Port Addresses

- Fixed I/O instruction uses an 8-bit I/O port address that on $A_{15}-A_0$ as 0000H–00FFH.
 - we often decode only address connections A_7-A_0 for an 8-bit I/O port address
- The DX register can also address I/O ports 00H–FFH.
- If the address is decoded as an **8-bit address**, we can never include I/O devices using a **16-bit address**.
 - the PC never uses or decodes an 8-bit address

- Figure 11–10 shows a **74ALS138 decoder** that decodes 8-bit I/O ports F0H - F7H.
 - identical to a **memory address** decoder except we only connect address bits A_7 – A_0 to the inputs of the decoder
- Figure 11–11 shows the PLD version, using a GAL22V10 (**a low-cost device**) for this decoder.
- The **PLD** is a better **decoder circuit** because the number of integrated circuits has been reduced to one device.

Figure 11–10 A port **decoder** that decodes 8-bit I/O ports. This decoder generates active low outputs for ports F0H–F7H.


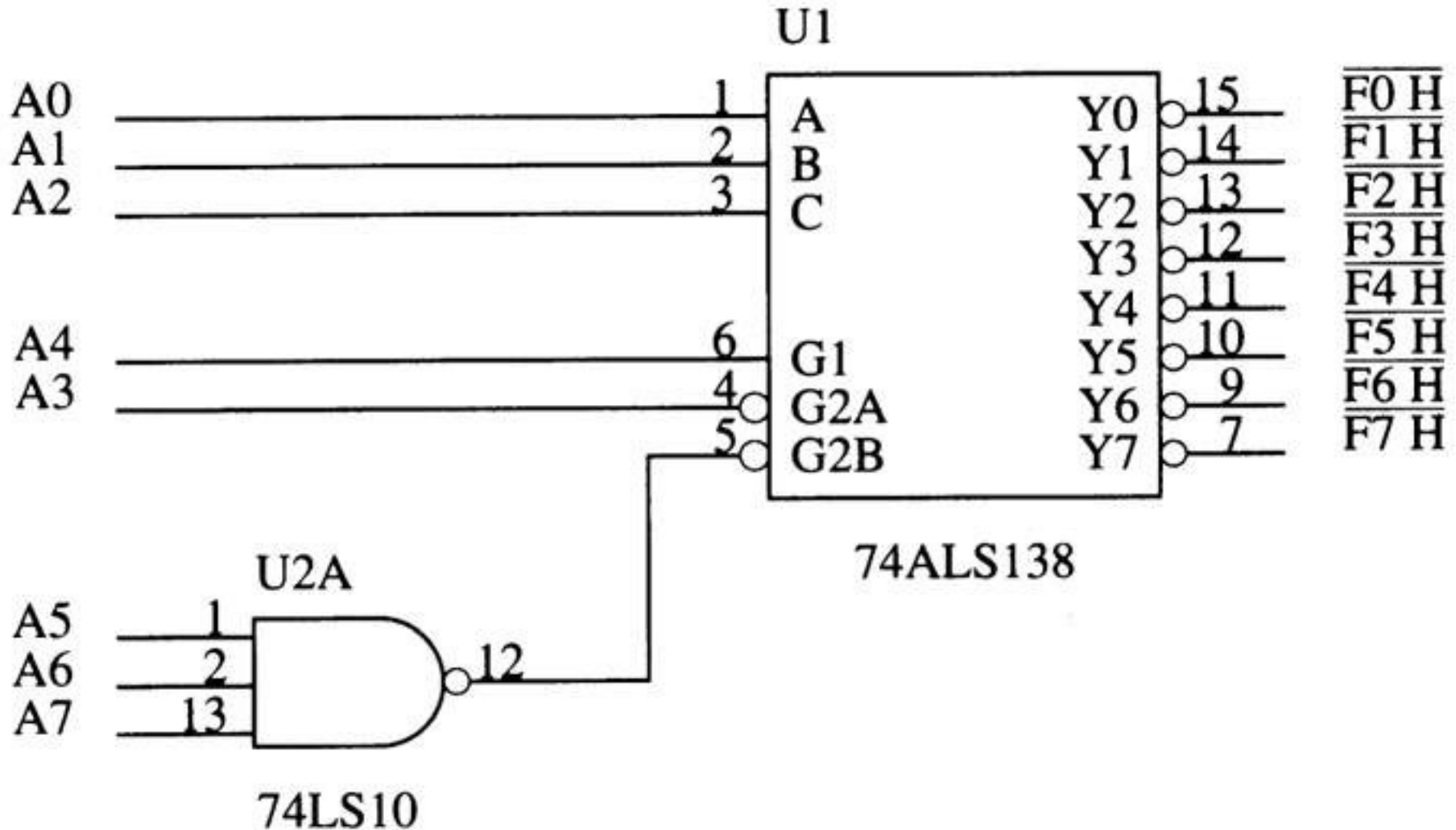



Figure 11–11 A PLD that generates part **selection** signals

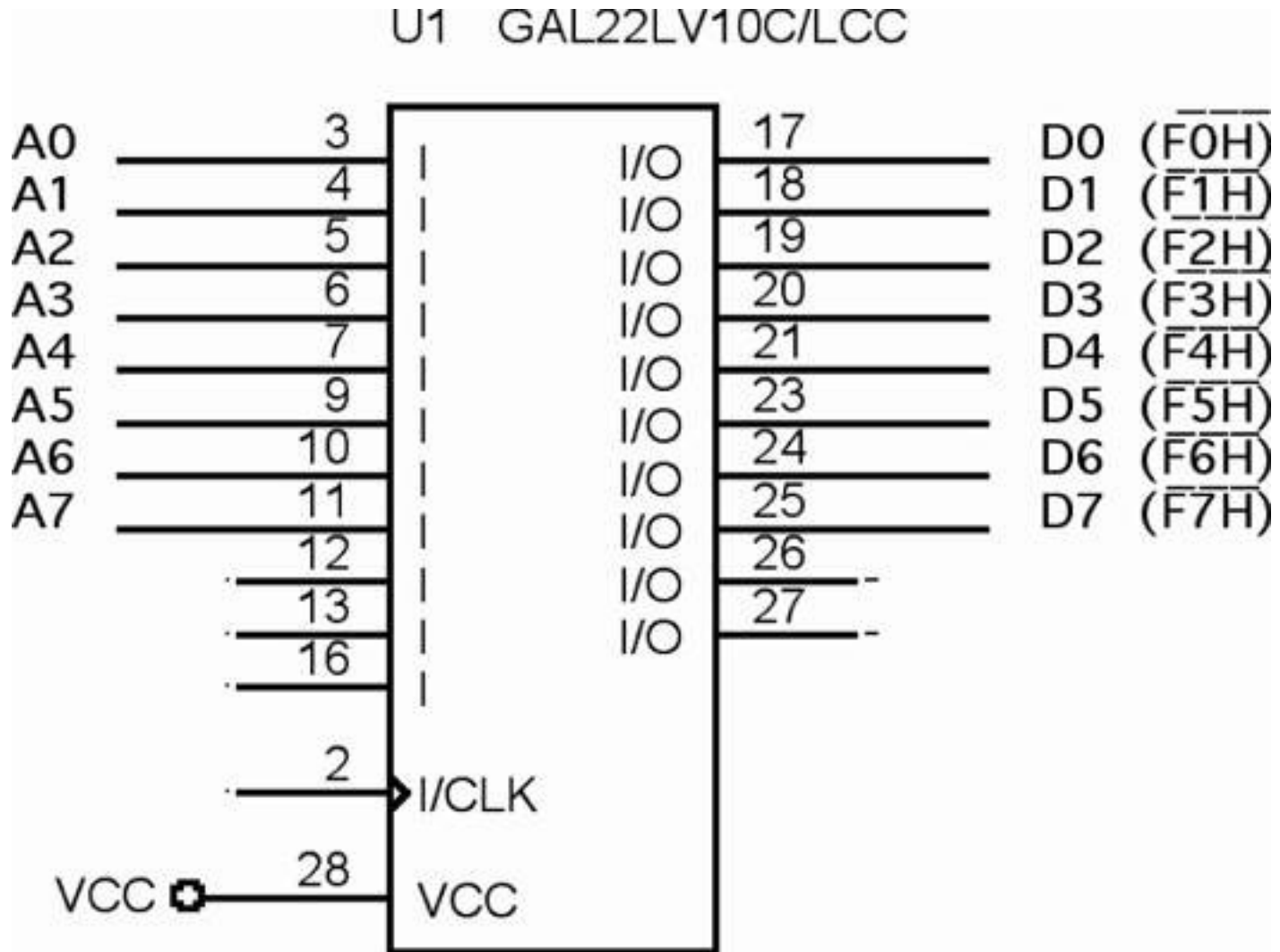

Decoding 16-Bit I/O Port Addresses

- PC systems typically use 16-bit I/O addresses.
 - 16-bit addresses rare in embedded systems
- The difference between decoding an 8-bit and a 16-bit I/O address is that eight additional address lines (A_{15} – A_8) must be decoded.
- Figure 11–12 illustrates a circuit that contains a PLD and a 4-input NAND gate used to decode I/O ports EFF8H–EFFFH.
- PLD generates address strobes for I/O ports


Figure 11–12 A PLD that **decodes** 16-bit I/O ports EFF8H through EFFFH.

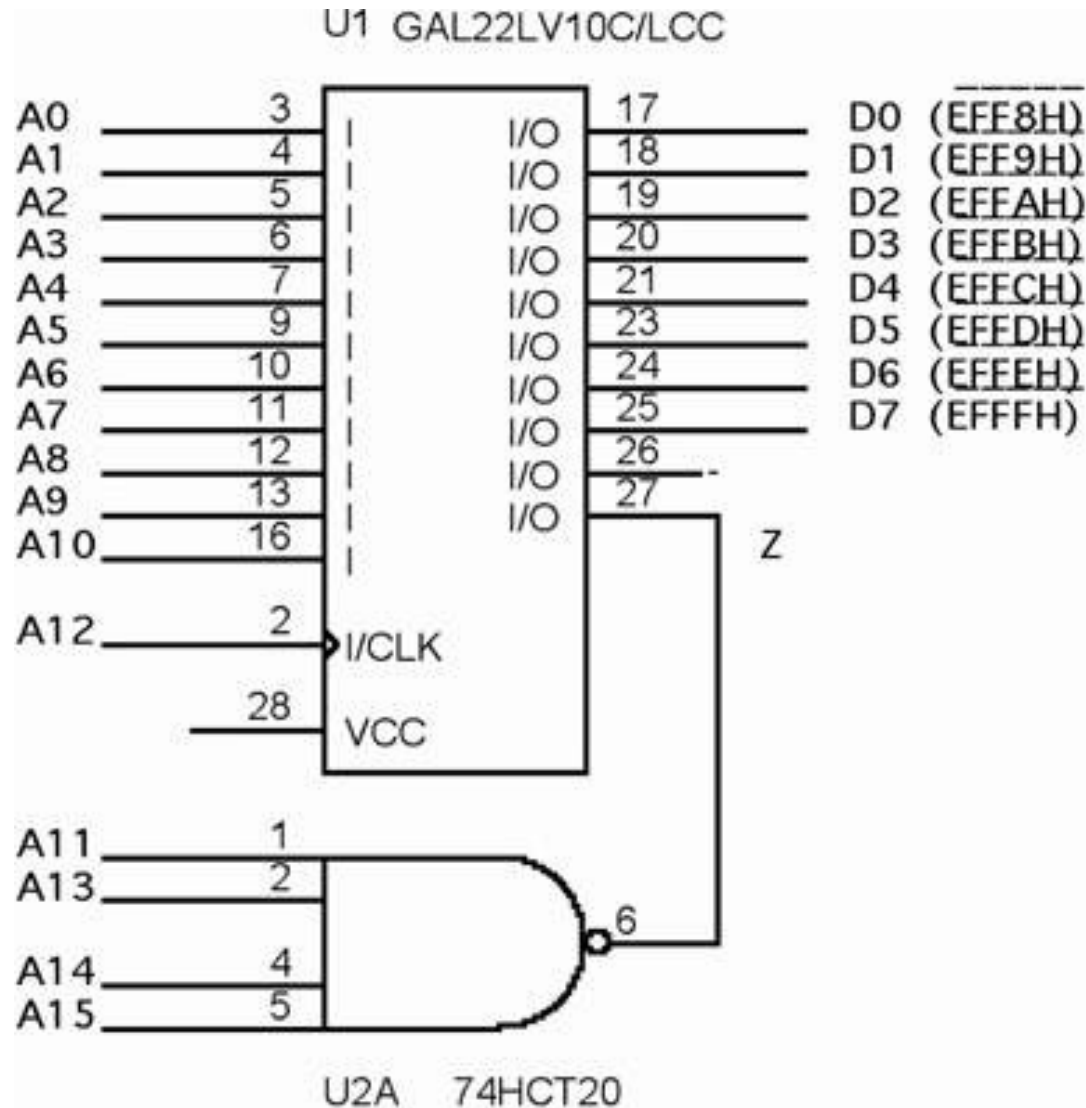

8- and 16-Bit Wide I/O Ports


- Data transferred to an 8-bit I/O device exist in one of the I/O banks in a **16-bit processor** such as 80386SX.
- The I/O system on such a microprocessor contains **two 8-bit memory banks**.
- Fig 11–13 shows separate **I/O banks** for a 16-bit system such as 80386SX.
- Because two I/O banks exist, any 8-bit I/O write requires a **separate write**.

Figure 11–13 The I/O banks found in the 8086, 80186, 80286, and 80386SX.

 

- I/O reads don't require **separate strobes**.
 - as with memory, the processor reads only the byte it expects and ignores the other byte
 - a read can cause problems when an I/O device responds incorrectly to a read operation
- Fig 11–14 shows a system with two different 8-bit output devices, located at 40H and 41H.
- These are 8-bit devices and appear in **different I/O banks**.
 - thus, separate I/O write signals are generated to clock **a pair of latches** that capture port data


Figure 11–14 An I/O port decoder that selects ports 40H and 41H for output data.

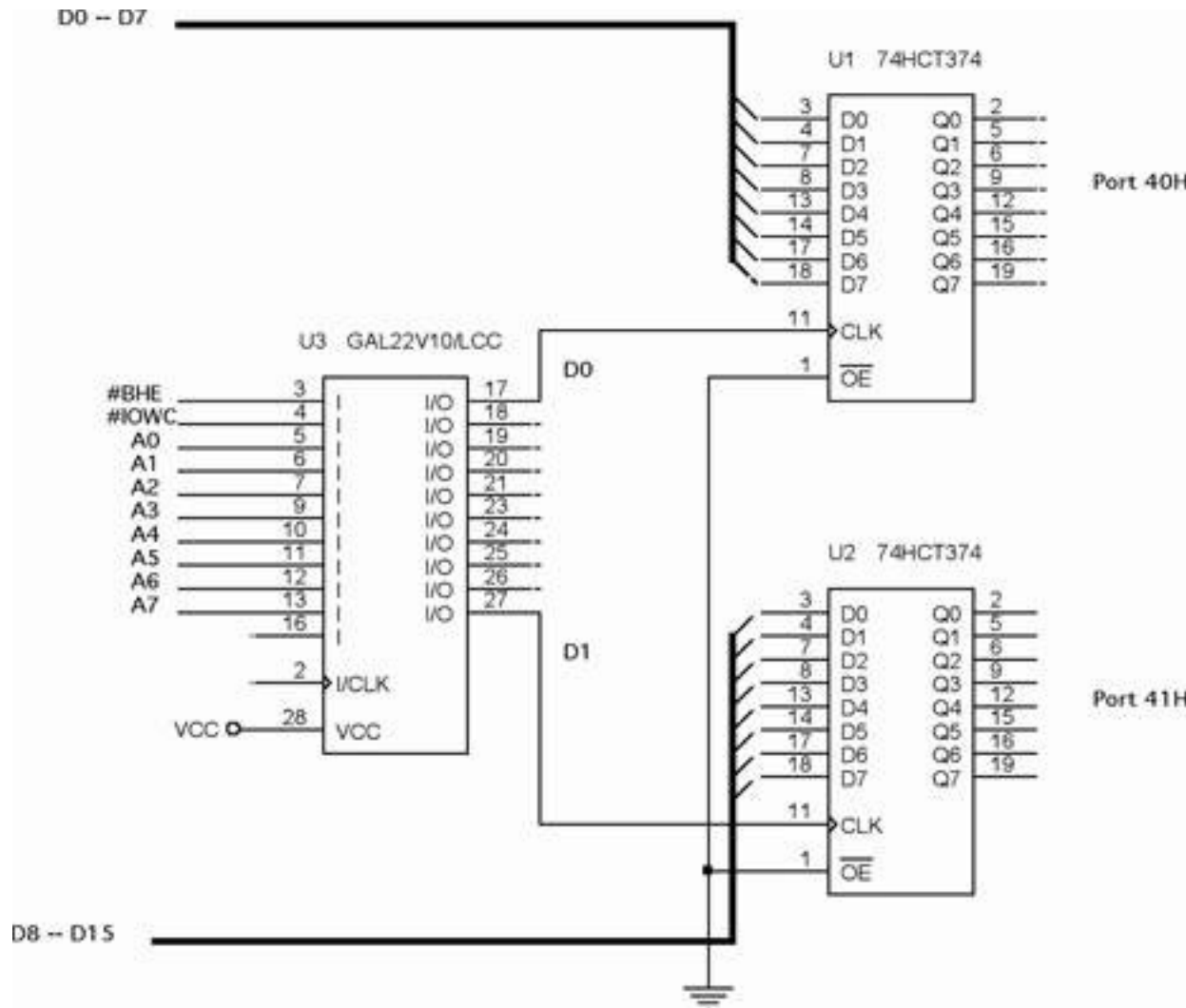

- all I/O ports use 8-bit addresses
- ports 40H & 41H can be addressed as **separate** 8-bit ports
- or as one 16-bit port

- Fig 11–15 shows a 16-bit device connected to function at 8-bit addresses 64H & 65H.
- The PLD decoder does not have a connection for address bits \overline{BLE} (A_0) and \overline{BHE} because the signals don't apply to 16-bit-wide devices.
- The program for the PLD, illustrated in Example 11–5, shows how the **enable signals** are generated for the **three-state buffers** (74HCT244) used as input devices.


Figure 11–15 A **16-bit-wide** port decoded at I/O addresses 64H and 65H.

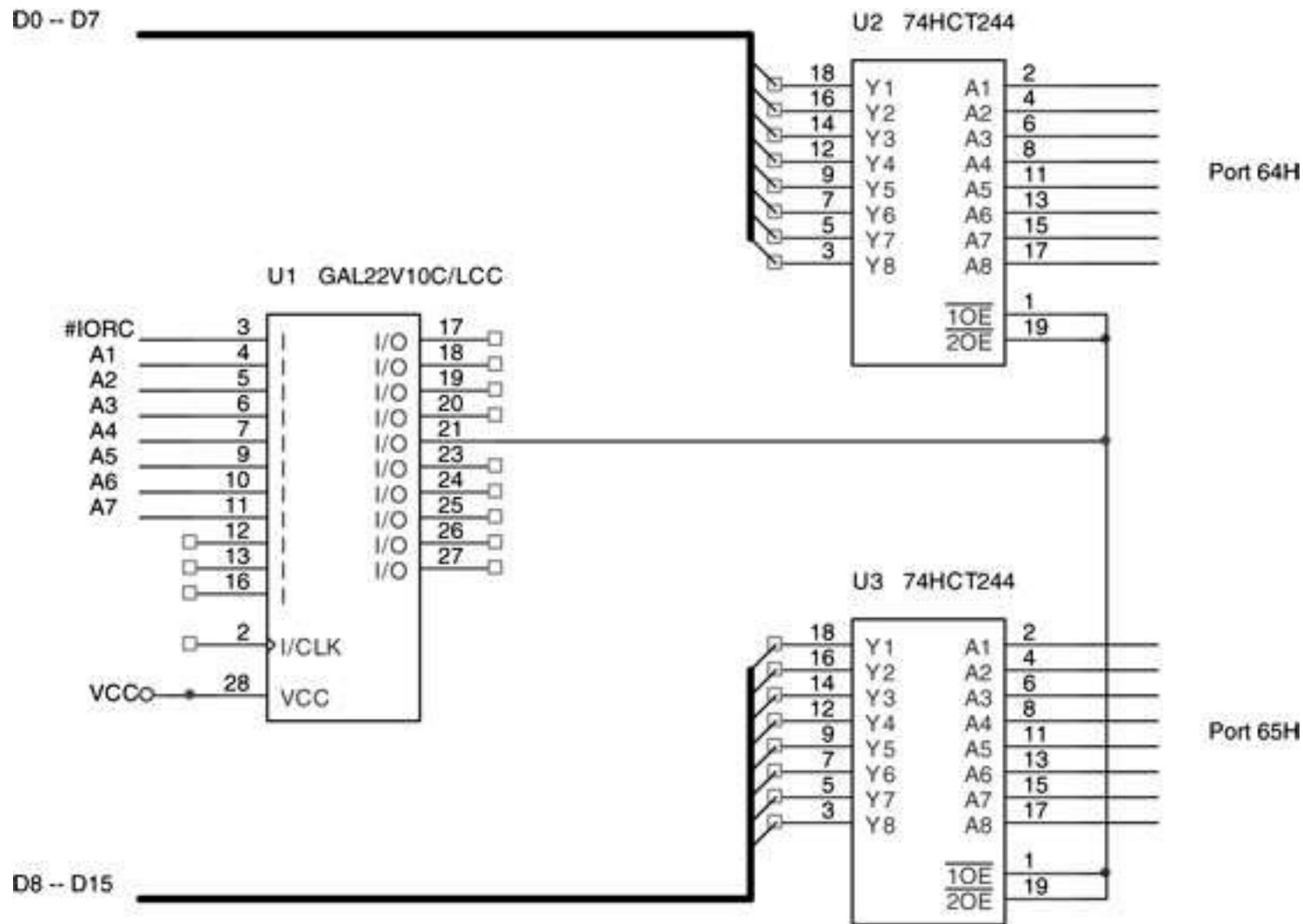

32-Bit-Wide I/O Ports

- May eventually become common because of **newer buses** found in computer systems.
- The EISA system bus supports **32-bit I/O** as well as the VESA local and current PCI bus.
 - not many I/O devices are 32 bits in width
- Fig 11–16 shows a **32-bit input port** for 80386DX - 80486DX microprocessor.
- The circuit uses a single PLD to decode the I/O ports and **four 74HCT244 buffers** to connect the I/O data to the data bus.

Figure 11–16 A **32-bit-wide port** decoded at 70H through 73H for the 80486DX microprocessor.

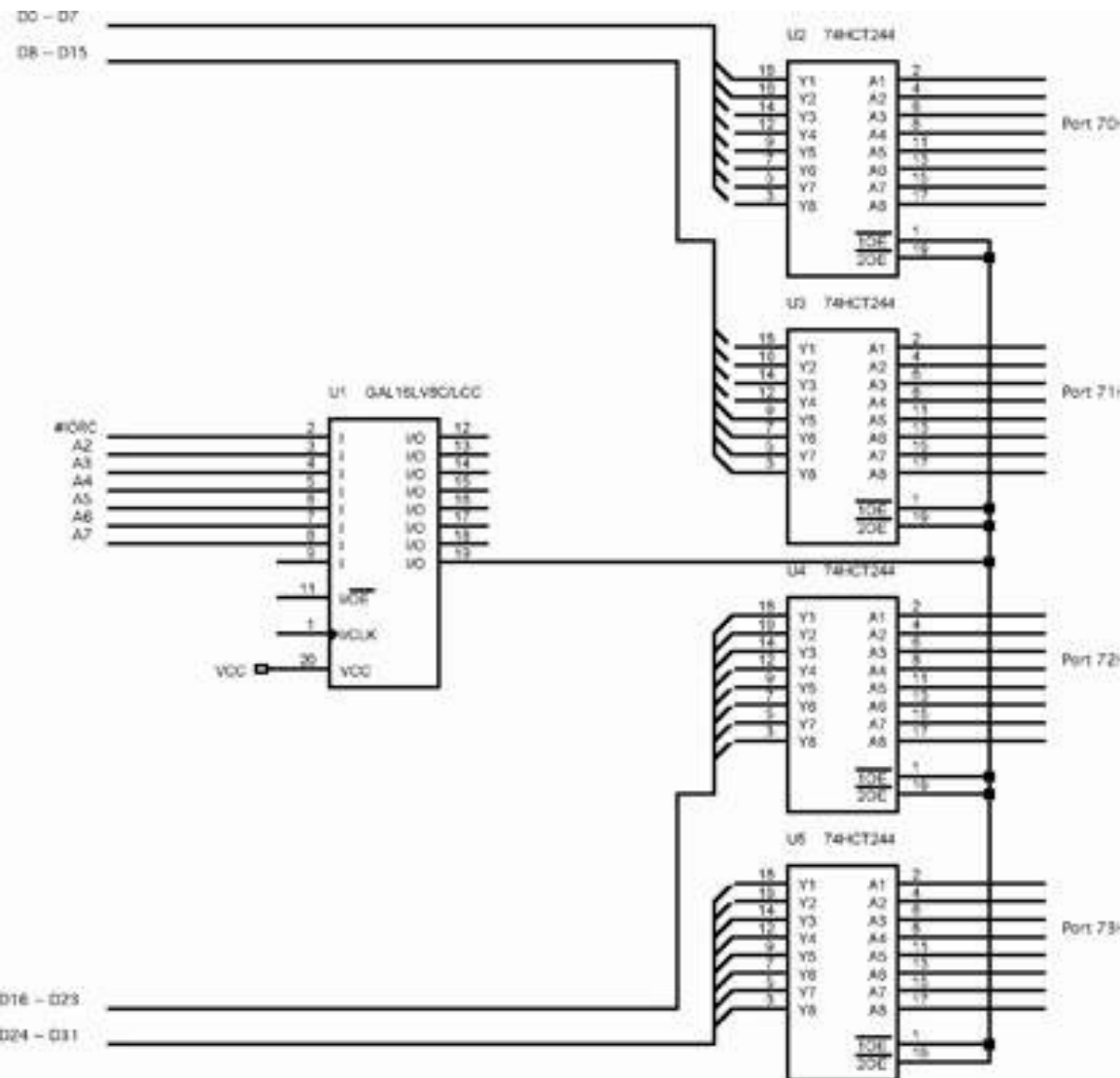


- I/O ports decoded by this interface are the 8-bit ports 70H–73H
- When writing to access this port, it is crucial to use the address 70H for 32-bit input
- as instruction `IN EAX, 70H`

- With the Pentium–Core2 and their **64-bit data buses**, I/O ports appear in various banks, as determined by the I/O port address.
- A 32-bit I/O access in the Pentium system can appear in any **four** consecutive I/O banks.
 - 32-bit ports 0100H–0103H appear in **banks 0–3**
- I/O **address range** must begin at a location where the **rightmost two bits are zeros**.
 - 0100H–0103H is allowable
 - 0101H–0104H is not

- Widest I/O transfers are **32 bits**, and there are no I/O instructions to support **64-bit transfers**.
 - true for Pentium 4 or Core2 in the 64-bit mode
- Suppose we need to interface a 16-bit-wide output port at I/O address 2000H and 2001H.
 - interface is illustrated in Figure 11–17
 - **PLD program** is listed in Example 11–7
- The problem that can arise is when the I/O port spans across a **64-bit boundary**.
 - example, a 16-bit- port at 2007H and 2008H

Figure 11–17 A Pentium 4 interfaced to a 16-bit-wide I/O port at port addresses 2000H and 2001H.

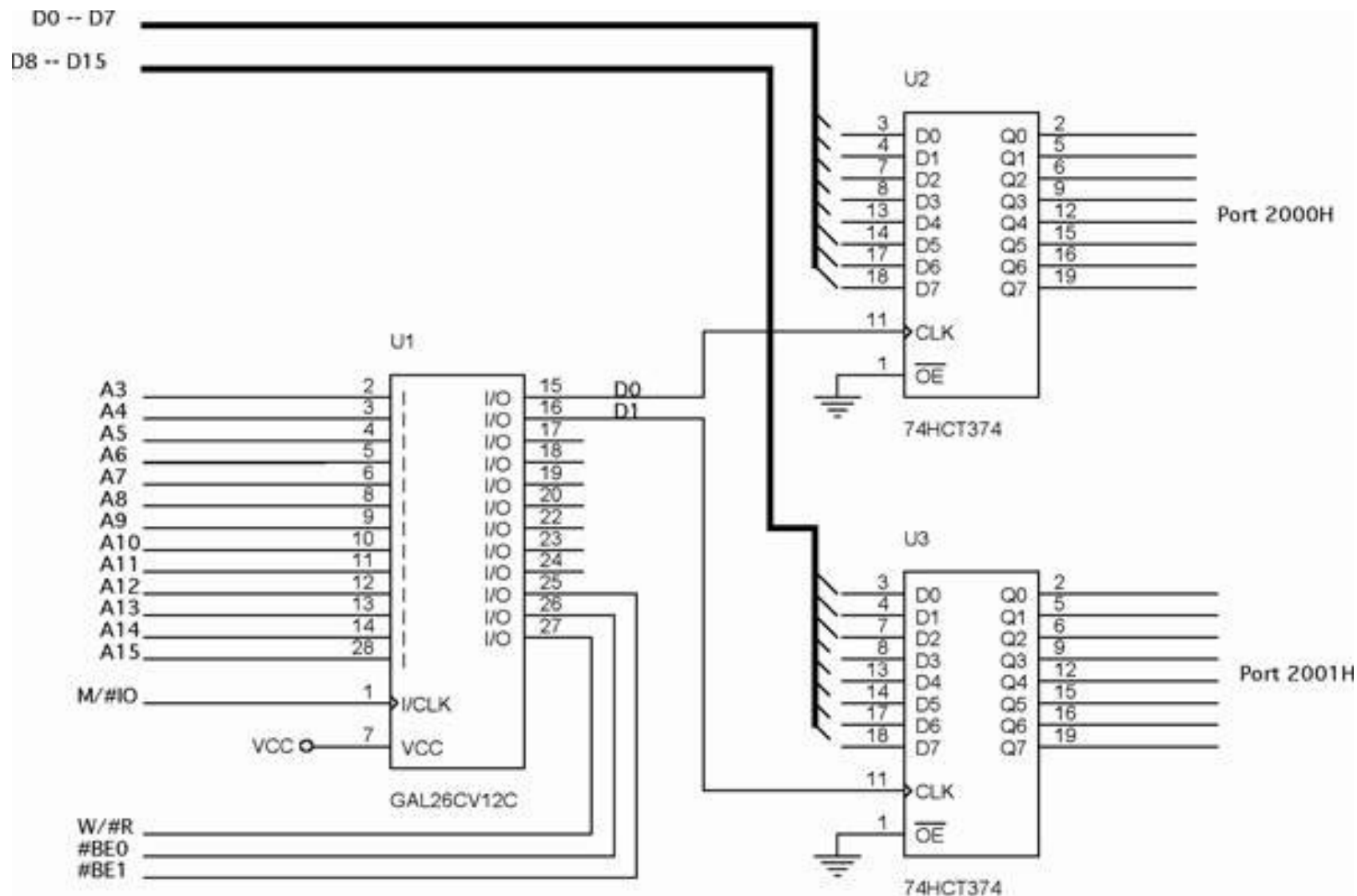

SUMMARY

- The 8086-Core2 microprocessors have two basic types of I/O instructions: IN and OUT.
- The IN instruction inputs data from an external I/O device into either the AL (8-bit) or AX (16-bit) register.
- The IN instruction is available as a fixed port instruction, a variable port instruction, or a string instruction (80286-Pentium 4) INSB or INSW.

SUMMARY

(*cont.*)

- The OUT instruction outputs data from AL or AX to an external I/O device and is available as a fixed, variable, or string instruction OUTSB or OUTSW.
- The fixed port instruction uses an 8-bit I/O port address, while the variable and string I/O instructions use a 16-bit port number found in the DX register.

SUMMARY

(*cont.*)

- Isolated I/O, sometimes called direct I/O, uses a separate map for the I/O space, freeing the entire memory for use by the program.
- Isolated I/O uses the IN and OUT instructions to transfer data between the I/O device and the micro-processor.

SUMMARY

(*cont.*)

- Memory-mapped I/O uses a portion of the memory space for I/O transfers.
- In addition, any instruction that addresses a memory location using any addressing mode can be used to transfer data between the microprocessor and the I/O device using memory-mapped I/O.

SUMMARY

(*cont.*)

- All input devices are buffered so that the I/O data are connected only to the data bus during the execution of the IN instruction.
- The buffer is either built into a programmable peripheral or located separately.
- All output devices use a latch to capture output data during the execution of the OUT instruction.

SUMMARY

(*cont.*)

- Handshaking or polling is the act of two independent devices synchronizing with a few control lines.
- This communication between the computer and the printer is a handshake or a poll.
- Interfaces are required for most switch-based input devices and for most output devices that are not TTL-compatible.

SUMMARY

(*cont.*)

- The I/O port number appears on address bus connections A7-A0 for a fixed port I/O instruction and on A15-A0 for a variable port I/O instruction (note that A15-A8 contains zeros for an 8-bit port).
- In both cases, address bits above A15 are undefined.

SUMMARY

(*cont.*)

- Because the 8086/80286/80386SX microprocessors contain a 16-bit data bus and the I/O addresses reference byte-sized I/O locations, I/O space is also organized in banks, as is the memory system.
- In order to interface an 8-bit I/O device to the 16-bit data bus, we often require separate write strobes (an upper and a lower) for I/O write operations.